

Chapter 3: Digital Systems and Logic Design

MCQs from the Chapter “Digital Systems and Logic Design”:

EXERCISE MCQs with Answers

1. Which of the following Boolean expressions represents the OR operation?

(a) AB (b) $A + B \checkmark$
 (c) A (d) AB

2. What is the dual of the Boolean expression $A \cdot 0 = 0$?

(a) $A + 1 = 1 \checkmark$ (b) $A + 0 = A$
 (c) $1 = A$ (d) $A * 0 = 0$

3. Which logic gate outputs true only if both inputs are true?

(a) OR gate (b) AND gate \checkmark
 (c) XOR gate (d) NOT gate

4. In a half-adder circuit, the carry is generated by which operation?

(a) XOR operation (b) AND operation \checkmark
 (c) OR operation (d) NOT operation

5. What is the decimal equivalent of the binary number 1101?

(a) 11 (b) 12
 (c) 13 \checkmark (d) 14

Final Answer Key:

1 \rightarrow (b) - 2 \rightarrow (a) - 3 \rightarrow (b) - 4 \rightarrow (b) - 5 \rightarrow (c)

Additional MCQs with Answers

Topic 1: Analog vs Digital Systems

1. Which of the following is an example of an analog system?

(a) Digital clock	(b) Thermometer with mercury <input checked="" type="checkbox"/>
(c) Calculator	(d) Computer
2. Digital systems use which type of signals?

(a) Continuous	(b) Discrete <input checked="" type="checkbox"/>
(c) Smooth	(d) Random
3. Which of the following is NOT an advantage of digital systems?

(a) Noise resistance	(b) High speed
(c) Infinite precision <input checked="" type="checkbox"/>	(d) Easy storage
4. Which system is better for processing audio signals directly?

(a) Digital system	(b) Analog system <input checked="" type="checkbox"/>
(c) Hybrid system	(d) None of these
5. Which of the following devices converts analog signals into digital form?

(a) Amplifier	(b) Digital clock
(c) ADC (Analog to Digital Converter) <input checked="" type="checkbox"/>	(d) Oscillator

Topic 2: Logic Gates (AND, OR, NOT, etc.)

1. The NOT gate is also known as:

(a) Inverter <input checked="" type="checkbox"/>	(b) Buffer
(c) Amplifier	(d) Subtractor
2. The symbol “.” in Boolean algebra represents:

(a) OR	(b) AND <input checked="" type="checkbox"/>
(c) NOT	(d) XOR
3. The output of an OR gate is 1 when:

(a) Both inputs are 0	(b) At least one input is 1 <input checked="" type="checkbox"/>
(c) Both inputs are 1 only	(d) Inputs are inverted
4. Which gate gives output 1 only if inputs are different?

(a) AND	(b) OR
(c) XOR <input checked="" type="checkbox"/>	(d) NOR
5. Which of the following is the universal gate?

(a) AND	(b) OR
(c) NAND <input checked="" type="checkbox"/>	(d) XOR

Topic 3: Truth Tables & Boolean Expressions

1. The truth table of an AND gate shows output 1 only when:

(a) One input is 1	(b) Both inputs are 1 <input checked="" type="checkbox"/>
(c) Both inputs are 0	(d) Inputs are different
2. The Boolean expression $A + A$ is equal to:

(a) $A \vee \vee$	(b) A^2
(c) $2A$	(d) 0
3. What is the result of $A \cdot 1$?

(a) 0	(b) 1
(c) $A \vee \vee$	(d) $A + 1$
4. The Boolean expression for a NOT gate is:

(a) $A + B$	(b) AB
(c) $A' \vee \vee$	(d) $A - B$
5. In Boolean algebra, the complement of 0 is:

(a) 0	(b) 1 <input checked="" type="checkbox"/>
(c) A	(d) A'

Topic 4: Logic Circuits & Half/Full Adder

1. A half-adder has:

(a) 1 input and 1 output	(b) 2 inputs and 2 outputs <input checked="" type="checkbox"/>
(c) 2 inputs and 1 output	(d) 3 inputs and 2 outputs
2. The sum output of a half-adder is produced by which gate?

(a) AND	(b) OR
(c) XOR <input checked="" type="checkbox"/>	(d) NOT
3. A full-adder has how many inputs?

(a) 2	(b) 3 <input checked="" type="checkbox"/>
(c) 4	(d) 1
4. A full-adder circuit can be made by combining:

(a) Two AND gates	(b) Two half-adders and an OR gate <input checked="" type="checkbox"/>
(c) Two XOR gates only	(d) One NAND and one NOR gate
5. Which component is most important in building arithmetic circuits in computers?

(a) Multiplexer	(b) Adder <input checked="" type="checkbox"/>
(c) Decoder	(d) Encoder

Topic 5: Applications of Digital Systems

1. Which of the following is a digital device?
(a) Analog thermometer (b) Digital camera
(c) Speedometer (needle type) (d) Mercury thermometer
2. Digital logic is used in:
(a) Traffic lights (b) Sundial
(c) Manual clock (d) Candle light
3. Which of the following uses digital signals?
(a) Computer (b) Analog radio
(c) Gramophone (d) Old telephone
4. In washing machines, digital logic is used for:
(a) Display only (b) Automatic control
(c) Heating only (d) None of these
5. Which field depends most heavily on digital systems?
(a) Agriculture (b) Medicine
(c) Handicrafts (d) Painting
