

## Chapter 3: Digital Systems and Logic Design

**Short Question from the Chapter “Digital Systems and Logic Design”:**

---

### EXERCISE Short Question with Answers

#### 1. Define a Boolean function and give an example.

**Ans:** A Boolean function is a function that gives output in **binary form (0 or 1)** depending on the values of input variables.

Example:  $F(A, B) = A + B$  (OR function) → output is 1 if at least one input is 1.

#### 2. What is the significance of the truth table in digital logic?

**Ans:** A truth table shows **all possible input combinations** and their corresponding output for a logic circuit or Boolean function.

It is important because it helps us **analyze, design, and verify** digital systems easily.

#### 3. Explain the difference between analog and digital signals.

**Ans:**

- **Analog signals:** Continuous signals that can take infinite values (e.g., sound waves, thermometer).
- **Digital signals:** Discrete signals that use only **0s and 1s** (e.g., computer data, digital clocks).

#### 4. Describe the function of a NOT gate with its truth table.

**Ans:** A NOT gate inverts the input. If the input is **1**, output becomes **0**; if input is **0**, output becomes **1**.

**Truth Table:**

**Input (A) Output (A')**

0	1
1	0

## 5. What is the purpose of a Karnaugh map in simplifying Boolean expressions?

**Ans:** A **Karnaugh map (K-map)** is a diagram used to **simplify Boolean expressions** by grouping 1s together.

It reduces **complex logic circuits** into simpler forms, saving cost and improving efficiency in digital design.

---

## Additional MCQs with Answers

---

### Topic 1: Analog and Digital Systems

**Q1.** What is the main limitation of analog signals?

**Ans.** Analog signals are easily affected by noise and distortion, which reduces accuracy. This makes them less reliable for data storage and transmission.

**Q2.** Why are digital systems preferred over analog systems?

**Ans.** Digital systems are more accurate, less affected by noise, and easier to process, store, and transmit.

**Q3.** What is quantization in digital systems?

**Ans.** Quantization is the process of converting continuous analog values into discrete digital values.

**Q4.** Give one real-life example of digital systems.

**Ans.** Mobile phones use digital systems for communication, storage, and processing.

**Q5.** What is the difference between discrete and continuous signals?

**Ans.** Discrete signals have separate values (like 0,1), while continuous signals change smoothly over time.

---

### Topic 2: Logic Gates

**Q1.** What is the function of an AND gate?

**Ans.** An AND gate outputs **1 only when all inputs are 1**; otherwise, the output is 0.

**Q2.** Why is a NOT gate called an inverter?

**Ans.** Because it reverses the input: if input = 1, output = 0, and if input = 0, output = 1.

**Q3.** Which gate is called a universal gate?

**Ans.** NAND and NOR gates are called universal gates because any logic circuit can be made using only them.

**Q4.** What is the truth table of an OR gate?

**Ans.** OR gate outputs 1 if **any input is 1**, and 0 only when all inputs are 0.

**Q5.** Give one real-life use of logic gates.

**Ans.** Logic gates are used in digital circuits like calculators and computer processors.

---

## Topic 3: Boolean Algebra

**Q1.** Who introduced Boolean algebra?

**Ans.** Boolean algebra was introduced by **George Boole** in the mid-19th century.

**Q2.** What are the basic operations of Boolean algebra?

**Ans.** The basic operations are **AND, OR, and NOT**.

**Q3.** Write one law of Boolean algebra.

**Ans.** Idempotent Law:  $A + A = A$  and  $A \times A = A$ .

**Q4.** Why is Boolean algebra important in digital logic?

**Ans.** It helps in analyzing and simplifying digital circuits.

**Q5.** What is the complement of a Boolean variable?

**Ans.** Complement means the opposite value: if  $A = 1$ ,  $A' = 0$ ; if  $A = 0$ ,  $A' = 1$ .

---

## Topic 4: Truth Tables

**Q1.** What is a truth table?

**Ans.** A truth table is a table that shows all possible input values and their corresponding output for a logic function.

**Q2.** How many rows will a truth table have for 3 inputs?

**Ans.** A truth table with 3 inputs will have  $2^3 = 8$  rows.

**Q3.** Why are truth tables important in digital design?

**Ans.** They help verify the working of a logic circuit for all possible inputs.

**Q4.** Can we use truth tables for Boolean simplification?

**Ans.** Yes, truth tables provide a clear way to analyze and simplify Boolean functions.

**Q5.** Give an example of a logic gate and its truth table.

**Ans.** NOT gate: Input 0 → Output 1; Input 1 → Output 0.

---

## Topic 5: Karnaugh Maps (K-Map)

**Q1.** What is a Karnaugh map?

**Ans.** A Karnaugh map is a diagram used to simplify Boolean expressions easily.

**Q2.** What is the minimum group size in K-Map?

**Ans.** The minimum group size is **2 cells** (1 cell is also allowed if no grouping possible).

**Q3.** What is the largest group size in a 4-variable K-map?

**Ans.** The largest group size is **16 cells** (covering the whole map).

**Q4.** Why are K-Maps used instead of Boolean algebra?

**Ans.** Because they are a faster and simpler method for minimization of logic expressions.

**Q5.** What are don't-care conditions in K-map?

**Ans.** Don't-care conditions represent inputs that never occur; they can be treated as 0 or 1 for simplification.

---